

Lecture 09: Datapath and Control

Topics

- Datapath
 - x stages performing computation [x=5]
 - y hardware components needed
- Combinational and Sequential logic
 - Logic Gates

SONGS ABOUT COMPUTER SCIENCE

DIGITAL LOGIC

Written by Emmanuel Schanzer
 To the tune of: A Spoonful of Sugar
http://www.cs.utexas.edu/users/walter/cs-songbook/digital_logic.html


To get all our programs to run
 There must be compilation done
 Into ones and zer-0s:
 Seems rather tame.

But how do ones and zeros make
 Our hardware bump and shake?
 Trans-...ls-...tor...gates!
 It won't be hard to see.
 We Use...


Digital logic: inputs, switches...and grounds.
 Inputs, switches...and grounds.
 Inputs, switches...and grounds.
 Just by abstracting voltage, into zer-0's and ones.
 We can hack all night and day.

Datapath Stages

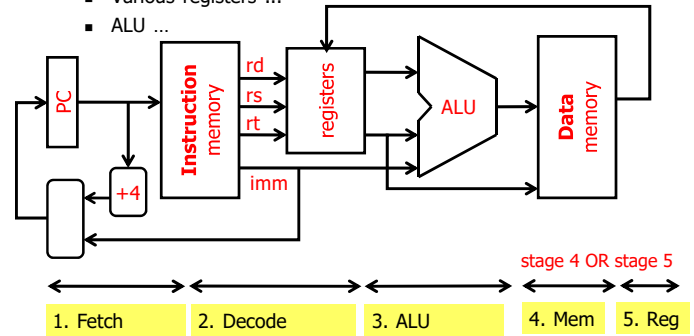- PC (Program Counter)...
- Memory...
- Various registers ...
- ALU ...



Five components of a Computer

 


- Processor (CPU):
 - Datapath: Elements that process data and addresses in the CPU [e.g. registers, ALUs, ...]
 - Control: Determines which computation is performed [e.g. Routes data thru datapath (which regs, which ALU op)]


Datapath Stages: 1

- There is a wide variety of MIPS instructions: what general steps do they have in common?

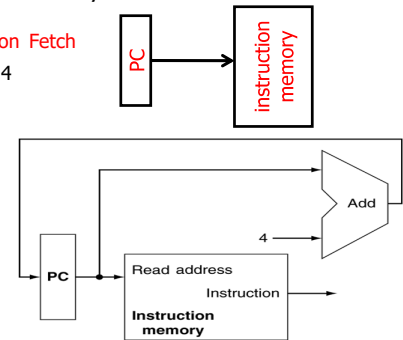Stage 1: Instruction Fetch
 $PC = PC + 4$



Connection and Communication via Bus

 


- A Bus is a shared communication link
- Single set of wires used to connect multiple subsystems
- A Bus is also a fundamental tool for composing large, complex systems
 - ... this topic is fully covered in Computer Architecture course...

Datapath Stages: 2


Stage 2: Instruction Decode [0x 02324020 --- refer to 'instruction decoding.pdf' in materials folder]

0x 02324020 - what MIPS instruction is it?																																
0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	21	22	23	24	25	26	27	28	29	30	31	
0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0		
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0		
op	rs	rt	rd	shamt	funct																											
0	0	0	0	0	0																											
R-type instruction						16	17	18	19	20	21	22	23	24	25	26	27	28	29	30	31											
						rd	rs	rt	shamt	funct																						
						0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
						add rd, rs, rt																										

 

Datapath concept


- Possible approach: build a single block to "execute an instruction", which designed to perform all necessary operations starting from fetching the instruction
 - Possible, but too bulky, inefficient and inflexible
- Modular approach: break up the process of "executing an instruction" into stages... datapath is born!
 - Advantages:
 - smaller, easier to understand and easier design blocks
 - easier to optimise: one block can be changed without affecting the others

 

Datapath Stages: 3


Stage 3: ALU (Arithmetic-Logic Unit)

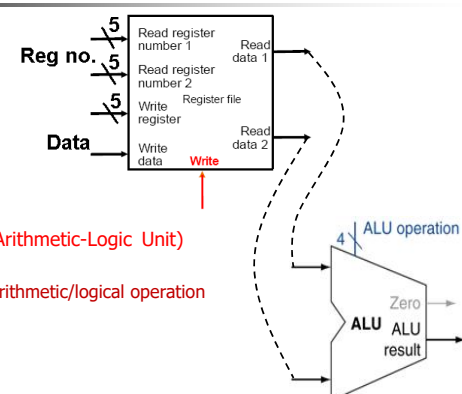- ...
- Perform arithmetic/logical operation
- ...




Datapath Stages: 4 and 5

Stage 4: Memory Access (load/store data)

 


Stage 5: Register Write

 


Branch Instructions

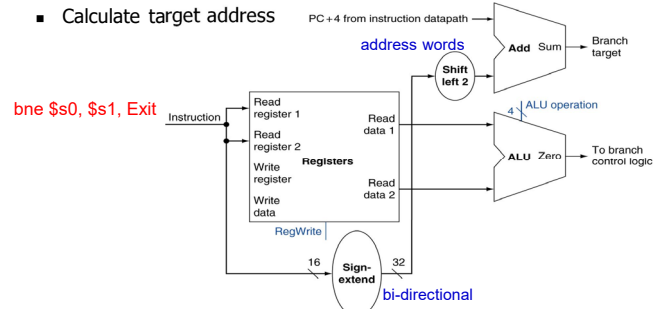- Read register operands
- Compare operands
 - Use ALU, subtract and check Zero output
- Calculate target address



Datapath Instruction Example

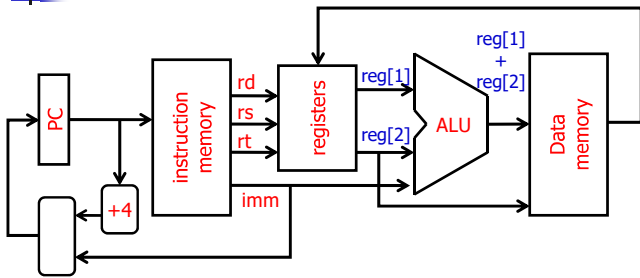

look at a sample instruction add: **add \$r3, \$r1, \$r2 # r3 = r1+r2**

Combinational and Sequential Circuits


- A complex functional component is implemented using lower level components - there are two classes of logic circuits:

COMBINATIONAL circuits	SEQUENTIAL/STATE circuits
No memory	Have internal memory (or: elements that contain state)
The output depends only on the input	<ul style="list-style-type: none"> the output depends both on the set of inputs supplied and the value stored in memory, which is called the state of the logic block how to ensure memory element is updated neither too soon, nor too late?
Truth Tables, Boolean Algebra	Finite state machine (Mealy, Moore)

- ...more on sequential circuits later, first: combinational logic...

Role of Controller

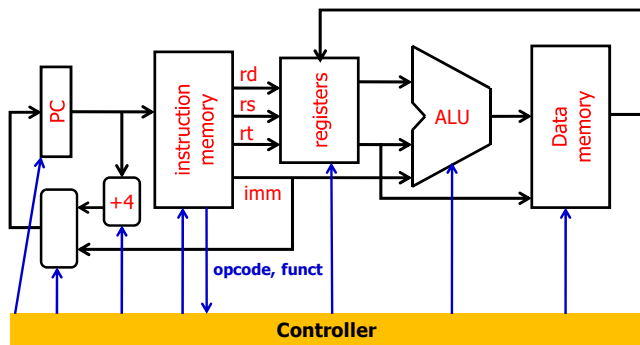- Controller causes the right transfers to happen.



Truth Tables, Boolean Algebra


- Combinational logic does not have memory, so it's described by defining the values of the outputs for each possible set of input values, as in **truth tables**.
- Another approach: one can express the logic function with logic equations with the use of **Boolean algebra**.

Main Boolean algebra laws: ["+" is operator OR, and "." is operator AND]

Identity law	$A+0=A$ and $A \cdot 1=A$
Zero and One laws	$A+1=1$ and $A \cdot 0=0$
Inverse laws	$A+\bar{A}=1$ and $A \cdot \bar{A}=0$
Commutative laws	$A+B=B+A$ and $A \cdot B=B \cdot A$
Associative laws	$A+(B+C)=(A+B)+C$ and $A \cdot (B \cdot C)=(A \cdot B) \cdot C$
Distributive laws	$A \cdot (B+C)=(A \cdot B)+ (A \cdot C)$ and $A+(B \cdot C)=(A+B) \cdot (A+C)$


R-Format Instructions

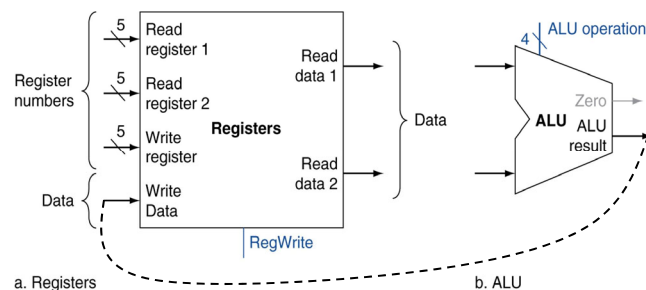- Read two register operands
- Perform arithmetic/logical operation
- Write register result



Logic Gates, Inverter and Multiplexor (Mux)

- AND gate ($c = a \cdot b$)

 

a	b	$c = a \cdot b$
0	0	0
0	1	0
1	0	0
1	1	1

- OR gate ($c = a + b$)




a	b	$c = a + b$
0	0	0
0	1	1
1	0	1
1	1	1

- Inverter ($c = \bar{a}$)



a	$c = \bar{a}$
0	1
1	0

 
- Multiplexor (Mux)
(if $d = 0$, $c = a$;
else $c = b$)



d	c
0	a
1	b

Selector (Decoder)


 
- Only one output is asserted for each input combination
- For example:
if inputs In0, In1, In2 are: **1 0 0** (decimal 4):
Out4 = **1**, all other outputs are **0**



Convert one bit-pattern to another bit-pattern


Multiplexor implementation [Exercise]

  - How to construct Multiplexor (**Mux**)?



Universal Gates [Exercise]

 - In fact ALL logic functions can be constructed with only a single gate type, if it is inverting.
- Common inverting gates are NOR (inverted OR) and NAND (inverted AND).
- NOR and NAND are called **universal gates**.



Exercise:
prove the above by implementing AND, OR and NOT:


A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

- using only NOR gates,
- using only NAND gates.

Arrays of logic elements

 
- Used when combinational operations need to be performed on entire word (32 bits)
 - for example when the result of an instruction that is written into a register can come from one of two sources



Universal Gates [Exercise]

 
Exercise:
prove the above by implementing AND, OR and NOT:

- using only NOR gates,
- using only NAND gates.





Programmable Logic Array (PLA)

 - Two-levels sum of products representation
 - the 1st stage: array of **AND** gates that forms a set of product terms (also known as *miniterms*),
 - the 2nd stage: array of **OR** gates each of which forms a logical sum of any number of the product terms.




XOR implementation [Exercise]

  - How to construct eXclusive OR (**XOR**)?



Sample PLA 1/2

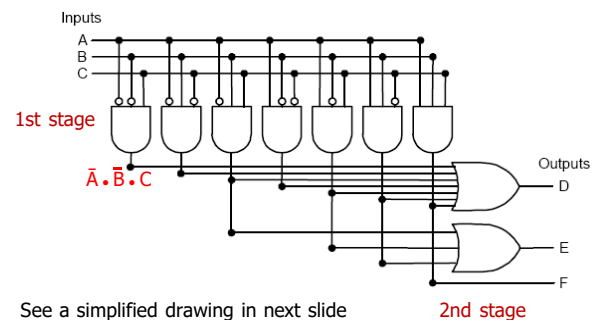- Implements logic from page C-13 in the textbook (three inputs, three outputs)




See a simplified drawing in next slide

2nd stage

Sample PLA 2/2

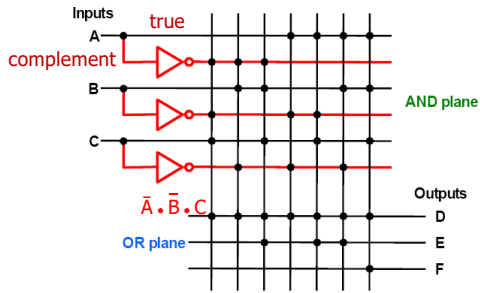- As before, simplified drawing shows AND and OR planes.
 - Note inputs A, B and C run the width of AND plane in both true and complement form.




Computer Organisation COMP2008, Jamie Yang: Lyang@westernsydney.edu.au

25

SR (set-reset) Latch, unlocked

 - SR-latch implemented with **NOR** Gates
- Output depends on both inputs and values stored (previous state)
 - $S = 1$ and $R = 1$ not allowed
 - $R=S=0$ (removal of the input combination of 0's and 1's), output will not change (NC) -- depends on the values in previous state
 - Otherwise output copying input (set or reset action)




Computer Organisation COMP2008, Jamie Yang: Lyang@westernsydney.edu.au

29

Clock

 - Clock: free running signal with fixed cycle time (clock period)




- Clock determines when to write memory element
 - level-triggered – act (store) on clock high (or low)
 - edge-triggered – act (store) only on clock edge
- We will consider here only negative (falling) edge-triggered clocking methodology

Computer Organisation COMP2008, Jamie Yang: Lyang@westernsydney.edu.au


26

D Latch (clocked), or: Delay Flip-Flop

 - When the clock C is asserted, the latch is opened, and the output Q immediately assumes the value of the D input
- Sometimes called a transparent latch (when the latch opened, Q changes as D changes)



 FYI - Electronics Demonstrations: "Clocked SR Flip-Flop" at <https://www.falstad.com/circuit/e-clockedsrff.html>



C controls the behavior of Q attempting to learn from D

Computer Organisation COMP2008, Jamie Yang: Lyang@westernsydney.edu.au

30

Clock in MIPS (5 steps of datapath)

- Synchronous (or clocked) combinational circuits
- Single-cycle machine: does everything in one clock cycle
 - instruction execution = up to 5 steps
 - must complete 5th step before cycle ends




Computer Organisation COMP2008, Jamie Yang: Lyang@westernsydney.edu.au


27

D flip-flop with a falling-edge trigger

 - Flip-flop: state changes only on a clock edge
 - Master: the first latch, when the clock C is asserted Q follows D
 - Slave: the second latch, when the clock C falls gets its input from the output of the master latch.



 FYI - Electronics Demonstrations: "Master-Slave Flip-Flop" at <https://www.falstad.com/circuit/e-masterslaveff.html>




C controls the behavior of Q attempting to learn from D

Computer Organisation COMP2008, Jamie Yang: Lyang@westernsydney.edu.au

31

Sequential logic: memory elements

 - All memory element store states:
 - The output from any memory element depends BOTH on the inputs and on the value stored inside the memory element.
- The simplest memory elements are unlocked (see S-R latch next).




Computer Organisation COMP2008, Jamie Yang: Lyang@westernsydney.edu.au

28


Register File Implementation

Appendix C, C-54

 - Register:** multiple flip-flops forming a single entity with the same clock signal



 - A register file with two read ports and one write port.
- Can be implemented with a decoder for each read or write port and an array of D flip-flops used as registers.




Computer Organisation COMP2008, Jamie Yang: Lyang@westernsydney.edu.au

32


Register File Implementation 1/2 (read)

 - Implementation of two register read ports for a 32-bit wide register file
- 'read register' signal used as the multiplexor selector signal.




Register File Implementation 2/2 (write)

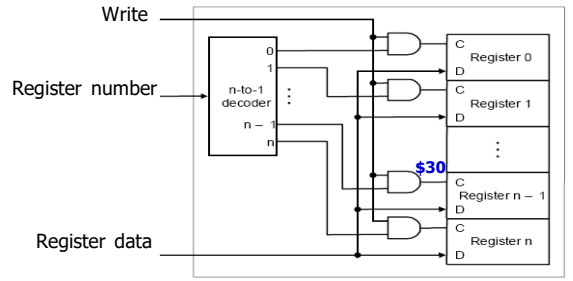- Decoder used together with the write signal to determine which register to write.
- All three inputs will have set-up and hold-time constraints.




Revision

 - The following block-diagram demonstrates the branch instruction processing. Explain what do 'Sign-extend' and 'Shift left 2' perform.



 - The two-stage Programmable Logic Array (PLA) models its output as "a sum of products". What does it mean?



Recommended readings

General Data	Unit Outline Learning Guide Teaching Schedule Aligning Assessments
Extra Materials	ascii_chart.pdf bias_representation.pdf HP_AopA2014-instruction_decoding.pdf masking_help.pdf PCSpim.pdf PCSpim Portable Version Library materials

PH6: Appendix B: The Basics of Logic Design
 PH5: Appendix B: The Basics of Logic Design
 PH4: Appendix C: The Basics of Logic Design

Text readings are listed in Teaching Schedule and Learning Guide

PH6 (PH5 & PH4 also suitable): check whether eBook available on library site
 PH6: companion materials (e.g. online sections for further readings)
<https://www.elsevier.com/books-and-journals/book-companion/9780128201091>
 PH5: companion materials (e.g. online sections for further readings)
<http://booksite.elsevier.com/978012407263/?ISBN=978012407263>