

SONGS ABOUT COMPUTER SCIENCE

...COMPUTER SCIENCE MAJOR?
 Written by Emmanuel Schanzer
 To the tune of: Hotel California
http://www.cs.utexas.edu/users/walter/cs-songbook/digital_logic.html

My mind is completely twisted
 My brain's completely snapped
 By these logic gates and Turing machines
 And those **Karnaugh maps**
 Registers dance in memory
 Clobbering the temps
 Some values you remember
 Some values you forget
 So I called up the professor
 Can I have more time?
 He said
 I haven't given an extension here since 1969

Topics

- Minimising Boolean expressions
 - Using Karnaugh maps
- ALU (Arithmetic Logic Unit)
- ALU design and implementation
 - 1-bit ALU
 - 32-bit ALU

Karnaugh maps: [I] State Sets

- State Sets for 2, 3 and 4-variable functions [**a'** stands for NOT a]

$2^2 = 4$ cases

$2^3 = 8$ cases

$2^4 = 16$ cases

Building blocks revisited

- We will build ALU using four hardware building blocks:

- AND gate** ($c = a \cdot b$)

a	b	c = a · b
0	0	0
0	1	0
1	0	0
1	1	1
- OR gate** ($c = a + b$)

a	b	c = a + b
0	0	0
0	1	1
1	0	1
1	1	1
- Inverter** ($c = \bar{a}$)

a	c = \bar{a}
0	1
1	0
- Multiplexor (Mux)**
 (if $d = 0$, $c = a$;
 else $c = b$)

d	c
0	a
1	b

Karnaugh maps: [II] Truth Table

- Truth Tables

- determined by the internal functions

$y_{AND} = y_0 \cdot ab + y_1 \cdot ab' + y_2 \cdot a'b + y_3 \cdot a'b'$
 $= 1 \cdot ab + 0 \cdot ab' + 0 \cdot a'b + 0 \cdot a'b'$
 $= ab$

$2^2 = 4$ cases $y = y_0 \cdot ab + y_1 \cdot ab' + y_2 \cdot a'b + y_3 \cdot a'b'$

Minimising Boolean expressions

- Before we start building ALU, consider how to minimise logic expressions in easy way, and implement circuits with as few logic gates as possible.
- For example, soon we will see that Carry Out formula expressed as **a sum of products** is (to be explained later):
 $CarryOut = (A' \cdot B \cdot CarryIn) + (A \cdot B' \cdot CarryIn) + (A \cdot B \cdot CarryIn) + (A' \cdot B' \cdot CarryIn)$

...happens to be equivalent of:

$CarryOut = (B \cdot CarryIn) + (A \cdot CarryIn) + (A \cdot B)$

- But: the above simplification is not immediately obvious.
- Logic minimising tool which we will use is known as:

Karnaugh maps.

Karnaugh maps: Simple mapping examples

- 2-input functions

$2^2 = 4$ cases

$y = y_0 \cdot ab + y_1 \cdot ab' + y_2 \cdot a'b + y_3 \cdot a'b'$

Karnaugh maps

- Product items: Minterms

$2^3 = 8$ cases

Sum of Products $y = y_0 \cdot abc' + y_1 \cdot abc + y_2 \cdot ab'c + y_3 \cdot ab'c' + \dots$

- Use **Truth Table** to determine y_0, y_1, \dots
- Use **Karnaugh maps** (or **K-maps**) to simplify the expression

Karnaugh maps: Grouping for simplification

- Rules of grouping:


- of 1s
- side by side

- Rules of simplification

"A change of one variable when crossing a horizontal or vertical boundaries of cells"


- Walk through a group
- Invariables survive; changed ones eliminated
- Sum of net results of all groups (clusters)**

 Karnaugh maps: Grouping for simplification




Build Logical Operations

 - ALU = { Logical Functions: AND, OR, ...
Arithmetic Operations: Adder, Subtraction
- FIRST: Logical Functions
 - the easiest to implement, they map directly into the hardware
 - 1-bit logical block for AND and OR:
 - Mux control line Operation=0 selects a AND b
 - Mux control line Operation=1 selects a OR b




Karnaugh maps: Grouping for simplification

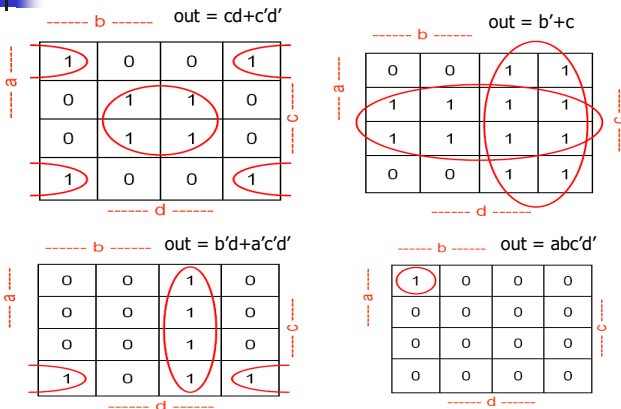

Build 1-bit Adder: Theory

 - Each bit of addition has
 - Three input bits: A_i , B_i , $CarryIn_i$
 - Two output bits: Sum_i , $CarryOut_i$
($CarryIn_{i+1} = CarryOut_i$)




How to build ALU [Arithmetic Logical Unit]

- 1-bit building blocks ready to implement, but MIPS word is 32 bits wide.

Solution:


- Build 32 separate 1-bit ALUs
- Build separate hardware blocks for each task
- Perform all operations in parallel
- Use a mux to chose operations

A cascaded view of 4-bit 'Full Adder'

 

Build 1-bit Adder: implementation

 
- Full adder, also called a (3,2) adder: 3 inputs and 2 outputs
- Half adder, also called (2,2) adder has only 2 inputs, a and b.




- STEPS to implement the adder:
 - Construct the circuit for Sum
 - Construct the circuit for CarryOut
 - Connect (1) and (2) together

More about muxes

 - Have **data** bits and **control** bits (data lines and control lines)
- Control bits select which data bit will pass through: all others are blocked
- In general:
 - 1 control bit selects between 2 data bits,
 - 2 control bits select between 4 data bits,
 - ...
 - n control bits select between 2^n data bits
- We can build a mux of any size to serve our purpose



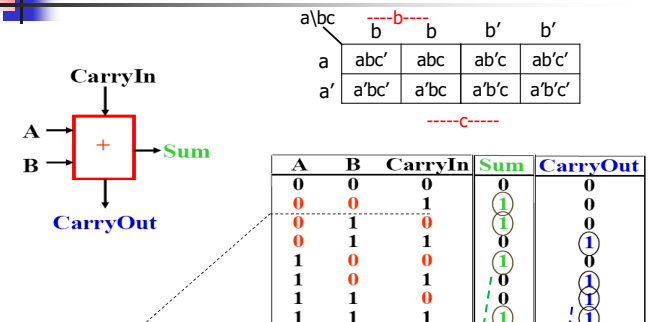1-bit Full Adder: truth table and formula



- Sum = $(A * B * CarryIn) + (A * B * CarryIn') + (A * B' * CarryIn) + (A * B' * CarryIn')$
- CarryOut = $(A * B * CarryIn) + (A * B * CarryIn') + (A * B' * CarryIn) + (A * B' * CarryIn')$

1-bit Full Adder: the Sum formula

- Can we simplify/minimise logic formulas for CarryOut and Sum for building the circuit using logic gates?
- Karnaugh table of the Sum formula: ... *grouping 1s*

a\bc	b	b'	b'
a	0	1	1
a'	1	0	0


No simplification possible

$$\text{Sum} = (A*B*CarryIn) + (A*B'*CarryIn) + (A*B*CarryIn) + (A*B*CarryIn)$$

a\bc	b	b'	b'
a	abc'	abc	ab'c
a'	a'bc'	a'bc	a'b'c

ALU: Adder and Logical operations

 - ALU = { Logical Functions: AND, OR, ... }
 { Arithmetic Operations: Adder, Subtraction }



A 1-bit ALU that performs AND, OR and Addition.

Mux "Operation" signal selects which operation is performed.

1-bit Full Adder: the CarryOut formula

- Karnaugh table of the CarryOut formula: ... *grouping 1s*

a\bc	b	b'	b'
a	1	1	0
a'	0	1	0

$(B*CarryIn) + (A*CarryIn) + (A*B)$

$$\text{CarryOut} = (A*B*CarryIn) + (A*B'*CarryIn) + (A*B*CarryIn) + (A*B*CarryIn)$$


$$= (B*CarryIn) + (A*CarryIn) + (A*B)$$

a\bc	b	b'	b'
a	abc'	abc	ab'c
a'	a'bc'	a'bc	a'b'c

Subtraction 1/3

- Subtraction: adding the negative version of an operand.
- Recall two's complement numbers: to create a negative number we need to:

- invert each bit of b
- add 1

 

Simply invert

How about 'add 1'?



1-bit Full Adder: formula -> circuit construction

- For Sum

$$\text{Sum} = (A*B*CarryIn) + (A*B'*CarryIn) + (A*B*CarryIn) + (A*B*CarryIn)$$

- For CarryOut

  
$$\text{CarryOut} = (B*CarryIn) + (A*CarryIn) + (A*B)$$



Digital circuit simulator: <https://circuitverse.org/>


Subtraction 2/3

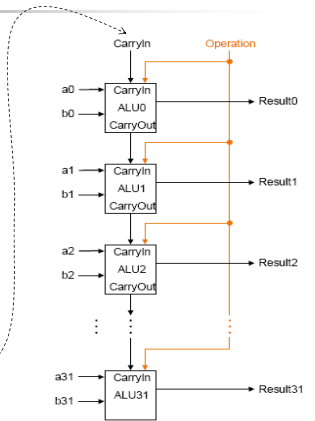- Notice that, the least significant bit still has CarryIn signal, which is never used for addition
- How CarryIn for ALU0 differs from other CarryIns?
- Initial CarryIn vs. Intermediate CarryIns.
- Initial CarryIn can be set at will
- If we set the Initial CarryIn bit to 1 instead of 0, we get: $a+b+1$



1-bit Full Adder: integrated circuit construction

- Connect Sum and CarryOut together

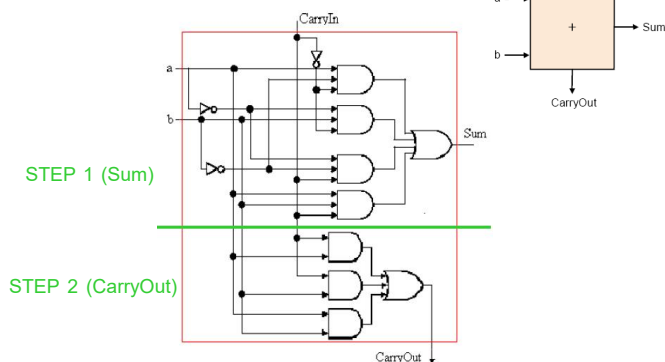


STEP 1 (Sum)


STEP 2 (CarryOut)

Subtraction 3/3

 - What happens if we now use Binvert for invert b and set the Initial CarryIn (at the least significant bit) to 1?
- The adder calculates: $a+\bar{b}+1 = a+(\bar{b}+1) = a+(-b)=a-b$
- This simplicity of hardware implementation of a two's complement adder is good illustration why two's complement representation is commonly used for integer computer arithmetics!



ALU structure so far

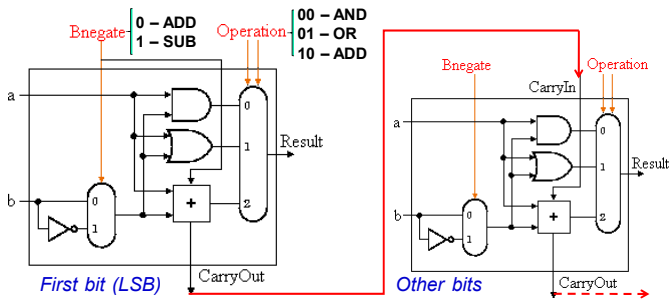


- Operations: AND OR ADD SUB
- Control lines: 000 001 010 110

Branch support

- Conditional branch instructions switch either if two registers are equal, or if they are not equal:
 - beq register1, register2, label (example: beq \$s4,\$s2, LABEL1)
 - bne register1, register2, label (example: bne \$s1,\$s3, L7)
- How to test that contents of two register is equal?
 - a = b means (a - b) = 0
- How to implement the above:
 - Subtract b from a
 - Add hardware to test if the result is zero
 - OR all the outputs together, and invert the output:


$$\text{Zero} = (\text{Result1} + \text{Result2} + \dots + \text{Result31})$$
 - variable $\begin{cases} 1 (\text{true}) & \text{if } (a - b) = 0 \text{ holds} \\ 0 (\text{false}) & \text{else} \end{cases}$
- Next slide show additional hardware for branch support :

32-bit ALU so far

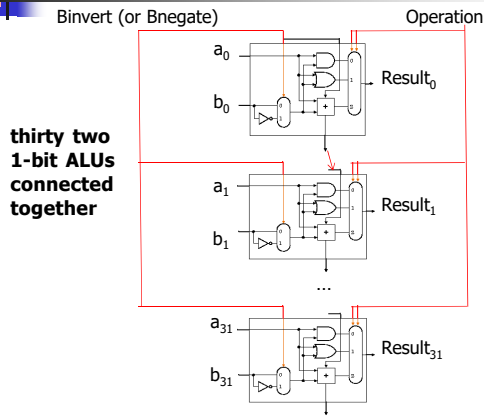

thirty two 1-bit ALUs connected together


32-bit ALU with branch support

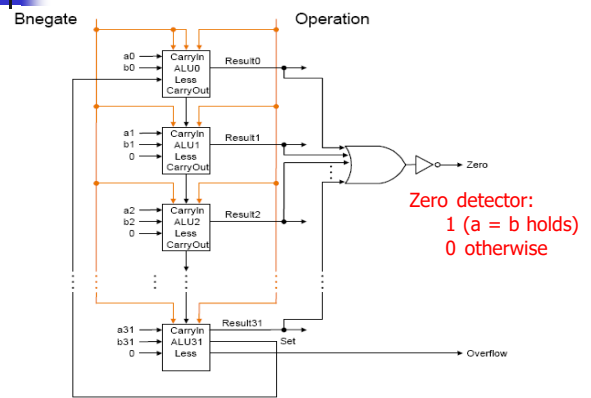

Set on less than (slt) support

- slt rd, rs, rt

 
$$rd := \begin{cases} 1 & \text{if } (rs < rt) \\ 0 & \text{else} \end{cases}$$




- Implement the idea in ALU
 - modify 1-bit ALU for the most significant bit (ALU31 for bit 31):
 - a new output line (**Set** - 1 bit) used only for slt
 - (by the way we added overflow detection logic, also associated with this bit)
 - new input line (**Less** - 32 bits) goes directly to mux
 - New control line (111) for slt

Shift instructions

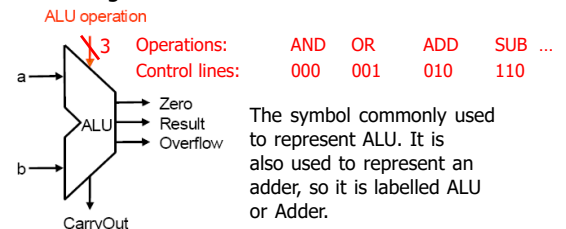- What is left:
 - logical and arithmetic shifts sll, srl, sra
 - Need a new data line for a shifter (L and R)?
 - however shifters are much more easily implemented outside the ALU.
- 1-bit ALU: integrated block notation





ALU with slt support

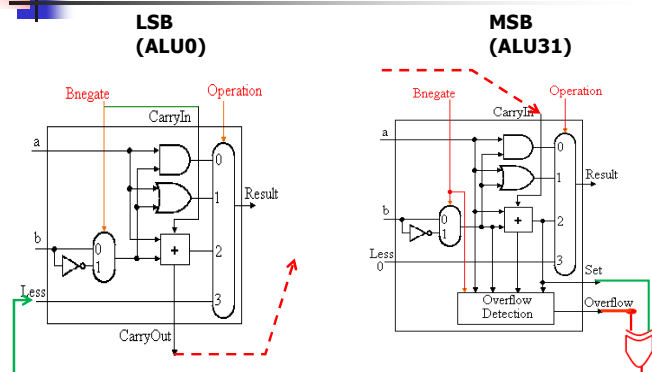

Revision and quiz

  - Given the following Karnaugh map. The output can be expressed by out = c'.
 - 1) True 2) False
- In 1-bit full Adder, the circuit construction for 'CarryOut' is correct:
 - 1) True 2) False
- How ALU is used to support the branch instruction?
 - beq register1, register2, label



Recommended readings

General Data	UnitOutline LearningGuide Teaching Schedule Aligning Assessments
Extra Materials	ascii_chart.pdf bias_representation.pdf HP_AppA.pdf instruction_decoding.pdf masking_help.pdf PCSpim.pdf PCSpim Portable Version Library materials

PH6: Appendix B: The Basics of Logic Design
PH5: Appendix B: The Basics of Logic Design
PH4: Appendix C: The Basics of Logic Design

Text readings are listed in Teaching Schedule and Learning Guide

PH6 (PH5 & PH4 also suitable): check whether eBook available on library site

PH6: companion materials (e.g. online sections for further readings)

<https://www.elsevier.com/books-and-journals/book-companion/9780128201091>

PH5: companion materials (e.g. online sections for further readings)

<http://booksite.elsevier.com/9780124077263/?ISBN=9780124077263>