

## Topics

- Minimising Boolean expressions
  - Using Karnaugh maps
- ALU (Arithmetic Logic Unit)
- ALU design and implementation
  - 1-bit ALU
  - 32-bit ALU

### SONGS ABOUT COMPUTER SCIENCE

#### *...COMPUTER SCIENCE MAJOR?*

Written by Emmanuel Schanzer

To the tune of: Hotel California

[http://www.cs.utexas.edu/users/walter/cs-songbook/digital\\_logic.html](http://www.cs.utexas.edu/users/walter/cs-songbook/digital_logic.html)

... ..

My mind is completely twisted

My brain's completely snapped

By these logic gates and Turing machines

And those **Karnaugh maps**

Registers dance in memory

Clobbering the temps

Some values you remember

Some values you forget

So I called up the professor

Can I have more time?

He said

I haven't given an extension here since 1969

... ..

# Building blocks revisited

- We will build ALU using four hardware building blocks:

1. **AND** gate ( $c = a \cdot b$ )




a	b	$c = a \cdot b$
0	0	0
0	1	0
1	0	0
1	1	1

2. **OR** gate ( $c = a + b$ )



a	b	$c = a + b$
0	0	0
0	1	1
1	0	1
1	1	1


3. **Inverter** ( $c = \bar{a}$ )

 

a	$c = \bar{a}$
0	1
1	0

 4. **Multiplexor (Mux)**

(if  $d = 0$ ,  $c = a$ ;  
else  $c = b$ )



d	c
0	a
1	b



# Minimising Boolean expressions

---

- Before we start building ALU, consider how to minimise logic expressions in easy way, and implement circuits with as few logic gates as possible.
- For example, soon we will see that Carry Out formula expressed as **a sum of products** is (to be explained later):

$$\text{CarryOut} = (A' * B * \text{CarryIn}) + (A * B' * \text{CarryIn}) + (A * B * \text{CarryIn}') + (A * B * \text{CarryIn})$$

...happens to be equivalent of:



$$\text{CarryOut} = (B * \text{CarryIn}) + (A * \text{CarryIn}) + (A * B)$$

- But: the above simplification is not immediately obvious.
- Logic minimising tool which we will use is known as:

**Karnaugh maps.**

# Karnaugh maps

- Product items: Minterms

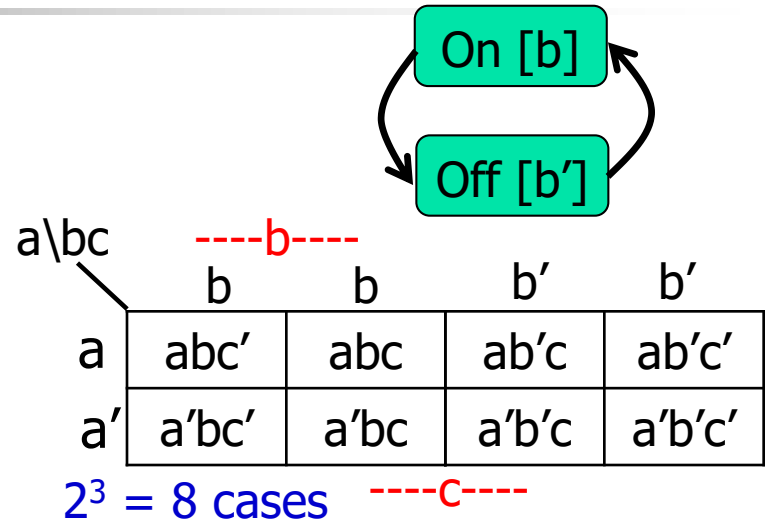 

- Sum of Products  $y = y_0 \cdot abc' + y_1 \cdot abc + y_2 \cdot ab'c + y_3 \cdot ab'c' + \dots$
- Use **Truth Table** to determine  $y_0, y_1, \dots$
- Use **Karnaugh maps** (or **K-maps**) to simplify the expression

# Karnaugh maps: [I] State Sets

- State Sets for 2, 3 and 4-variable functions [**a'** stands for **NOT a**]



a\b	b	b'
a	ab	ab'
a'	a'b	a'b'

$2^2 = 4$  cases

a\bc	<b>-----b-----</b> b	b	b'	b'
a	abc'	abc	ab'c	ab'c'
a'	a'bc'	a'bc	a'b'c	a'b'c'


$2^3 = 8$  cases **-----c-----**

ac\b	<b>-----b-----</b> b	b	b'	b'
<b>-----a-----</b> a	abc'd'	abc'd	ab'c'd	ab'c'd'
<b>-----a-----</b> a	abcd'	abcd	ab'cd	ab'cd'
	a'bcd'	a'bcd	a'b'cd	a'b'cd'
	a'bc'd'	a'bc'd	a'b'c'd	a'b'c'd'

$2^4 = 16$  cases **-----d-----**
 
# Karnaugh maps: [II] Truth Table

- Truth Tables
  - determined by the internal functions



a\b [State Set]


	b	b'
a	ab	ab'
a'	a'b	a'b'

$$\begin{aligned}
 Y_{\text{AND}} &= y_0 \cdot ab + y_1 \cdot ab' + y_2 \cdot a'b + y_3 \cdot a'b' \\
 &= 1 \cdot ab + 0 \cdot ab' + 0 \cdot a'b + 0 \cdot a'b' \\
 &= ab
 \end{aligned}$$

$2^2 = 4$  cases  $y = y_0 \cdot ab + y_1 \cdot ab' + y_2 \cdot a'b + y_3 \cdot a'b'$

# Karnaugh maps: Simple mapping examples

- 2-input functions

 

a\b [State Set]

	b	b'
a	ab	ab'
a'	a'b	a'b'

$2^2 = 4$  cases

$$y = y_0 \cdot ab + y_1 \cdot ab' + y_2 \cdot a'b + y_3 \cdot a'b'$$

	b	b'
a	0	0
a'	0	0

What logic function is that?  
out=0

	b	b'
a	1	1
a'	1	1

What logic function is that?  
out=1


	b	b'
a	1	1
a'	0	0

What logic function is that?  
out=ab+ab'  
out=a(b+b')  
out=a

# Karnaugh maps: Grouping for simplification

- Rules of grouping:

- of 1s
- side by side

 

- Rules of simplification

“A change of one variable when crossing a horizontal or vertical boundaries of cells”

- Walk through a group
- Invariables survive; changed ones eliminated
- Sum of net results of all groups (clusters)**



# Karnaugh maps: Grouping for simplification

ac\b/d

	-----b-----			
	b	b	b'	b'
-----a-----	abc'd'	abc'd	ab'c'd	ab'c'd'
a	abcd'	abcd	ab'cd	ab'cd'
a	a'bcd'	a'bcd	a'b'cd	a'b'cd'
	a'bc'd'	a'bc'd	a'b'c'd	a'b'c'd'

-----c-----

$2^4 = 16$  cases -----d-----

-----b-----

out = b'

0	0	1	1
0	0	1	1
0	0	1	1
0	0	1	1

-----d-----

-----c-----

-----b-----

out = a'c'

0	0	0	0
0	0	0	0
0	0	0	0
1	1	1	1

-----d-----

-----c-----

-----a-----

-----b-----

out = c'

1	1	1	1
0	0	0	0
0	0	0	0
1	1	1	1

-----d-----

-----c-----

-----a-----

# Karnaugh maps: Grouping for simplification

----- b ----- out =  $cd + c'd'$

1	0	0	1
0	1	1	0
0	1	1	0
1	0	0	1

----- d -----

----- b ----- out =  $b' + c$

0	0	1	1
1	1	1	1
1	1	1	1
0	0	1	1

----- d -----

----- b ----- out =  $b'd + a'c'd'$

0	0	1	0
0	0	1	0
0	0	1	0
1	0	1	1

----- d -----

----- b ----- out =  $abc'd'$

1	0	0	0
0	0	0	0
0	0	0	0
0	0	0	0

----- d -----

# How to build ALU [Arithmetic Logical Unit]

- 1-bit building blocks ready to implement, but MIPS word is 32 bits wide.
- Solution:



Build 32 separate 1-bit ALUs

Build separate hardware blocks for each task

Perform all operations in parallel


Use a mux to chose operations

## A cascaded view of 4-bit 'Full Adder'

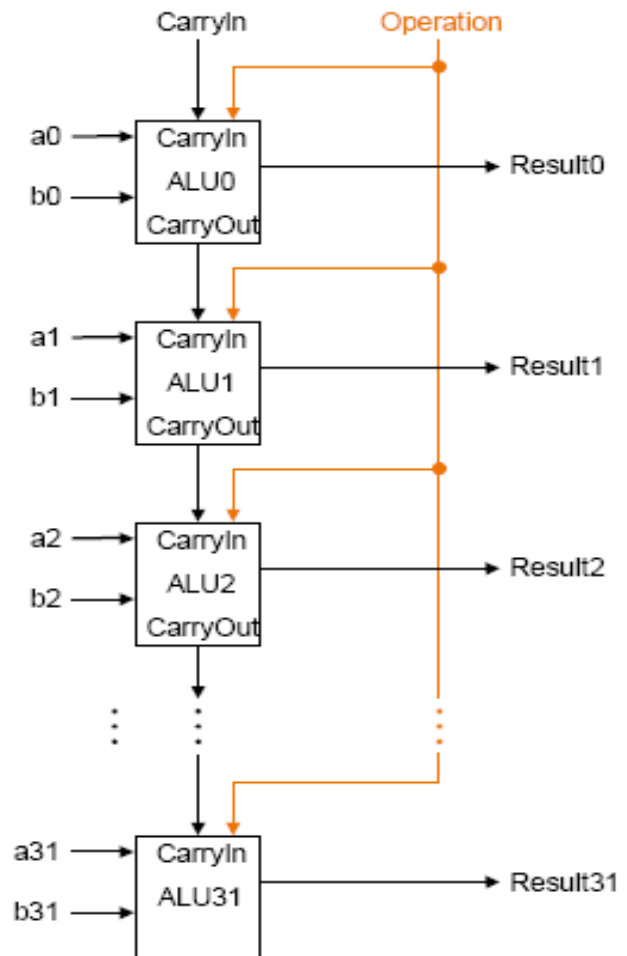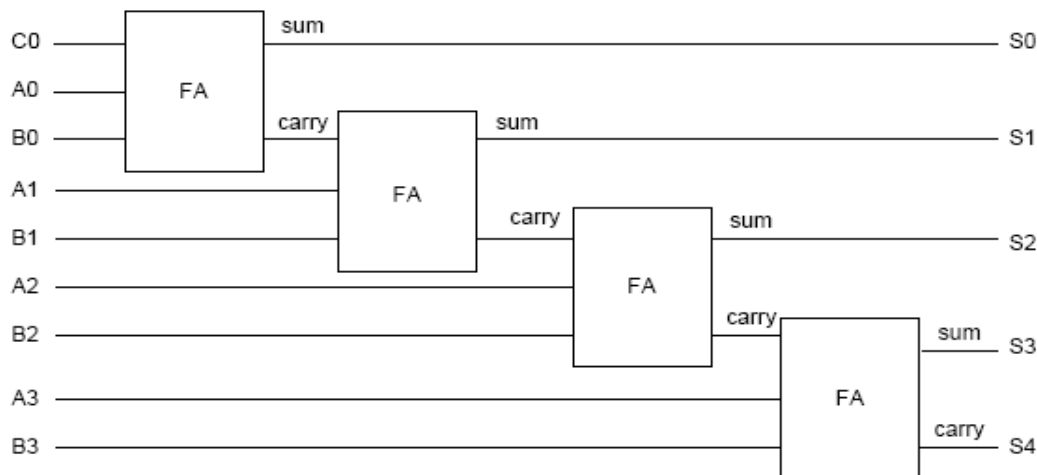

 
# More about muxes

- Have **data** bits and **control** bits (data lines and control lines )
- Control bits select which data bit will pass through: all others are blocked
- In general:
  - 1 control bit selects between 2 data bits,
  - 2 control bits select between 4 data bits,
  - . . . .
  - n control bits select between  $2^n$  data bits
- We can build a mux of any size to serve our purpose



 
# Build Logical Operations

- ALU =  $\left\{ \begin{array}{l} \text{Logical Functions: AND, OR} \\ \text{Arithmetic Operations} \left\{ \begin{array}{l} \text{Adder} \\ \text{Subtraction} \end{array} \right. \end{array} \right. \dots \dots$
- FIRST: Logical Functions
  - the easiest to implement, they map directly into the hardware
  - 1-bit logical block for AND and OR:
    - Mux control line Operation=0 selects a AND b
    - Mux control line Operation=1 selects a OR b



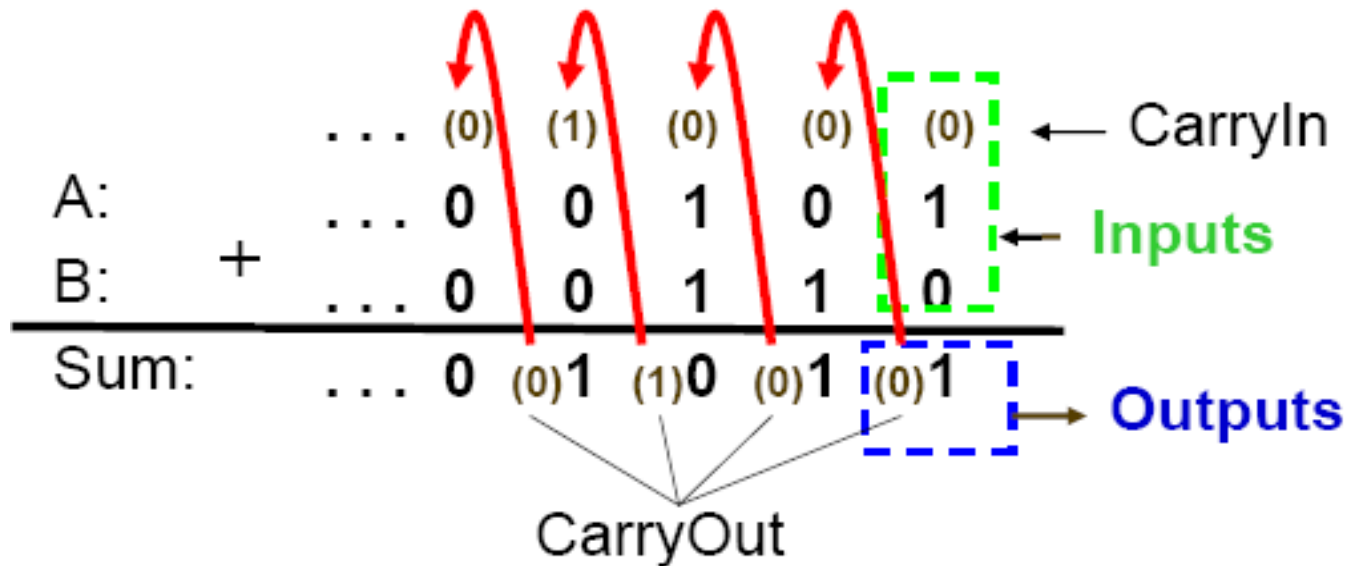
# Build 1-bit Adder: Theory

- Each bit of addition has
  - Three input bits:  $A_i$   $B_i$   $CarryIn_i$
  - Two output bits:  $Sum_i$   $CarryOut_i$   
(  $CarryIn_{i+1} = CarryOut_i$  )



 
# Build 1-bit Adder: implementation

- Full adder, also called a (3,2) adder: 3 inputs and 2 outputs
- Half adder, also called (2,2) adder has only 2 inputs, a and b.



- STEPS to implement the adder:
  1. Construct the circuit for Sum
  2. Construct the circuit for CarryOut
  3. Connect (1) and (2) together
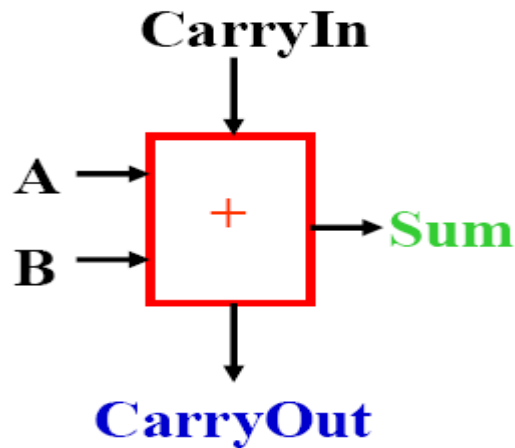
# 1-bit Full Adder: truth table and formula



a\bc	<del>---b---</del>	b	b'	b'
a	abc'	abc	ab'c	ab'c'
a'	a'bc'	a'bc	a'b'c	a'b'c'

-----C-----

A	B	CarryIn	Sum	CarryOut
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- **Sum** =  $(A' * B' * \text{CarryIn}) + (A' * B * \text{CarryIn}') + (A * B' * \text{CarryIn}') + (A * B * \text{CarryIn})$
- **CarryOut** =  $(A' * B * \text{CarryIn}) + (A * B' * \text{CarryIn}) + (A * B * \text{CarryIn}') + (A * B * \text{CarryIn})$



# 1-bit Full Adder: the Sum formula

- Can we simplify/minimise logic formulas for CarryOut and Sum for building the circuit using logic gates?
- Karnaugh table of the Sum formula: ... *grouping 1s*

a\bc	$\overset{\text{-----}b\text{-----}}{b}$	$b$	$b'$	$b'$
a	0	1	0	1
a'	1	0	1	0

**No  
simplification  
possible**

$\text{-----}c\text{-----}$

$$\text{Sum} = (A' * B' * \text{CarryIn}) + (A' * B * \text{CarryIn}') + (A * B' * \text{CarryIn}') + (A * B * \text{CarryIn})$$

a\bc	$\overset{\text{-----}b\text{-----}}{b}$	$b$	$b'$	$b'$
a	$abc'$	<b>abc</b>	$ab'c$	<b>ab'c'</b>
a'	<b>a'bc'</b>	$a'bc$	<b>a'b'c</b>	$a'b'c'$

# 1-bit Full Adder: the CarryOut formula

- Karnaugh table of the CarryOut formula: ... *grouping 1s*

a\bc	-----b-----		b'	b'
	b	b	b'	b'
a	1	1	1	0
a'	0	1	0	0
	-----c-----			

$$(B * \text{CarryIn}) + (A * \text{CarryIn}) + (A * B)$$

## CarryOut

$$= (A' * B * \text{CarryIn}) + (A * B' * \text{CarryIn}) + (A * B * \text{CarryIn}') + (A * B * \text{CarryIn})$$


$$= (B * \text{CarryIn}) + (A * \text{CarryIn}) + (A * B)$$

	b	b	b'	b'
a	<b>abc'</b>	<b>abc</b>	<b>ab'c</b>	ab'c'
a'	a'bc'	<b>a'bc</b>	a'b'c	a'b'c'
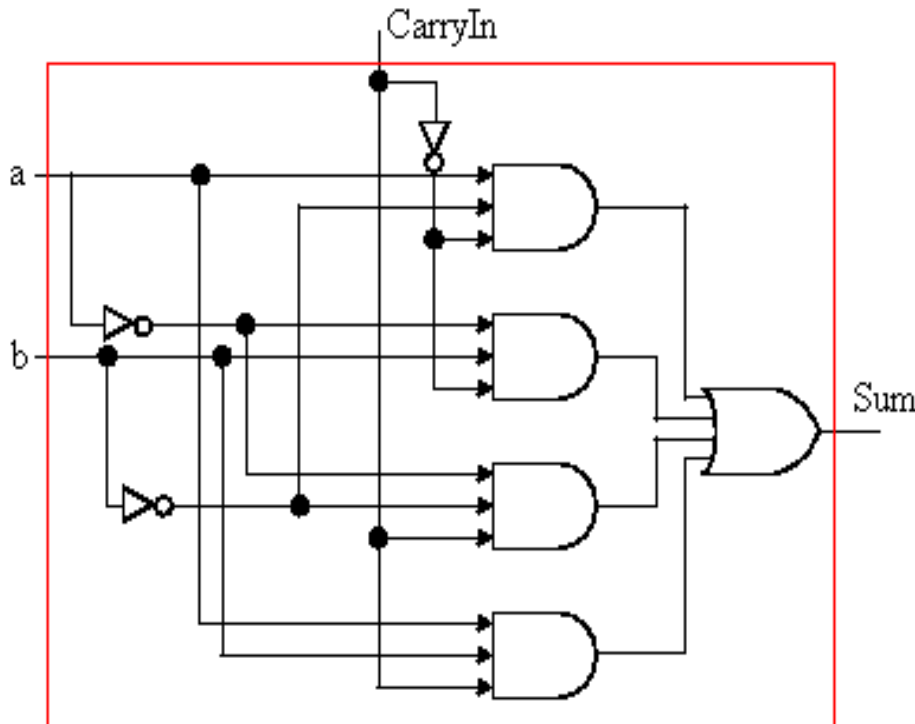
# 1-bit Full Adder: formula -> circuit construction


- For Sum

$$\text{Sum} = (A * B * \text{CarryIn}) + (A * B * \text{CarryIn}') + (A * B' * \text{CarryIn}') + (A * B * \text{CarryIn})$$



- For CarryOut


 
$$\text{CarryOut} = (B * \text{CarryIn}) + (A * \text{CarryIn}) + (A * B)$$



Digital circuit simulator:  
<https://circuitverse.org/>

# 1-bit Full Adder: integrated circuit construction


- Connect Sum and CarryOut together

  

# ALU: Adder and Logical operations

- ALU = 

{	Logical Functions: AND, OR	{	...
	Arithmetic Operations		Adder Subtraction

 


A 1-bit ALU that performs AND, OR and Addition.

Mux "Operation" signal selects which operation is performed.

# Subtraction 1/3

- Subtraction: adding the negative version of an operand.
- Recall two's complement numbers: to create a negative number we need to:

1. invert each bit of  $b$
2. add 1

 


Simply invert

How about 'add 1' ?


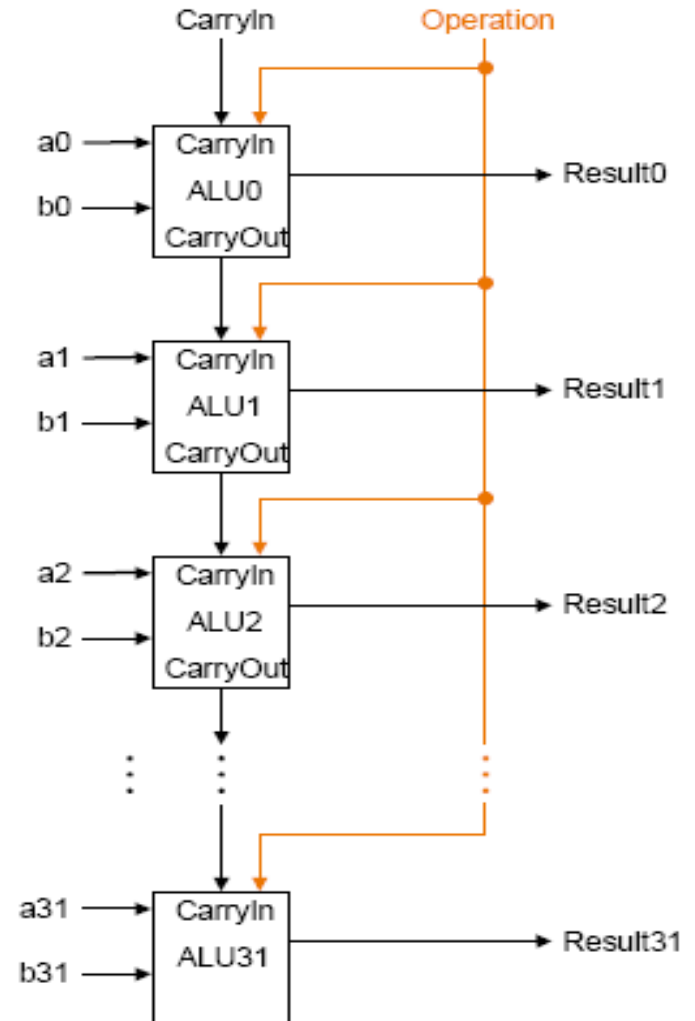
# Subtraction 2/3

- Notice that, the least significant bit still has CarryIn signal, which is never used for addition
- How CarryIn for ALU0 differs from other CarryIns?
  - Initial CarryIn vs. Intermediate CarryIns.
  - Initial CarryIn can be set at will
- If we set the Initial CarryIn bit to 1 instead of 0, we get:  $a+b+1$



 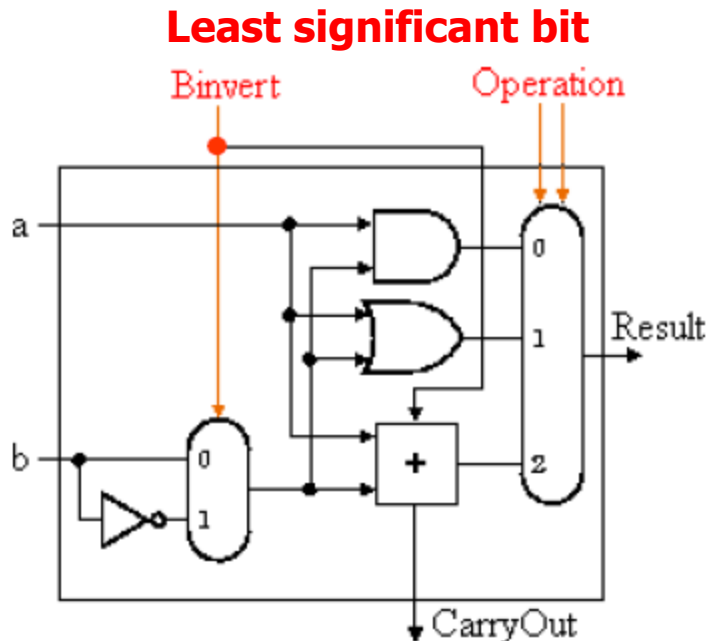
# Subtraction 3/3

- What happens if we now use Binvert for invert b and set the Initial CarryIn (at the least significant bit) to 1?
  - The adder calculates:  $a + \bar{b} + 1 = a + (\bar{b} + 1) = a + (-b) = a - b$
- This simplicity of hardware implementation of a two's complement adder is good illustration why two's complement representation is commonly used for integer computer arithmetics!





# ALU structure so far

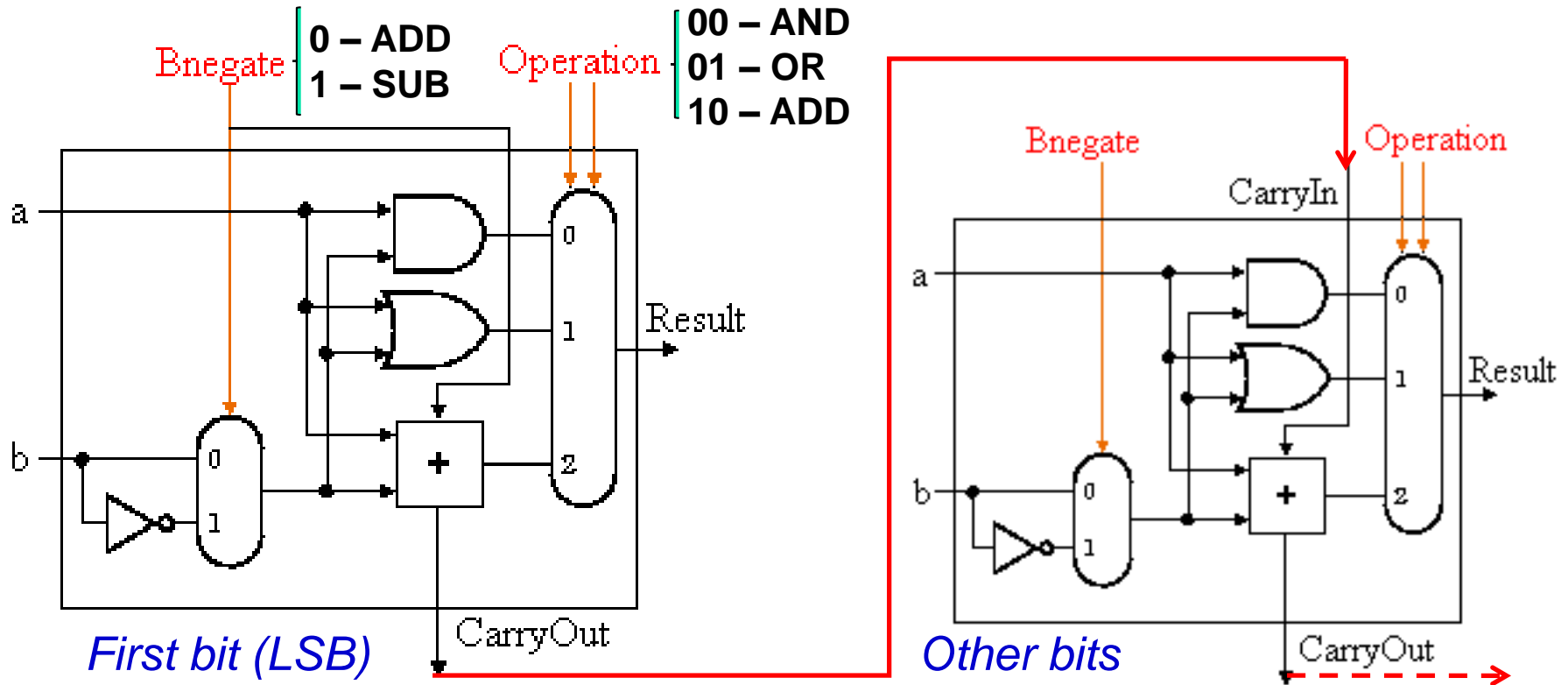


- Operations: AND OR ADD SUB
- Control lines: 000 001 010 110

# 32-bit ALU so far

Binvert (or Bnegate)

Operation

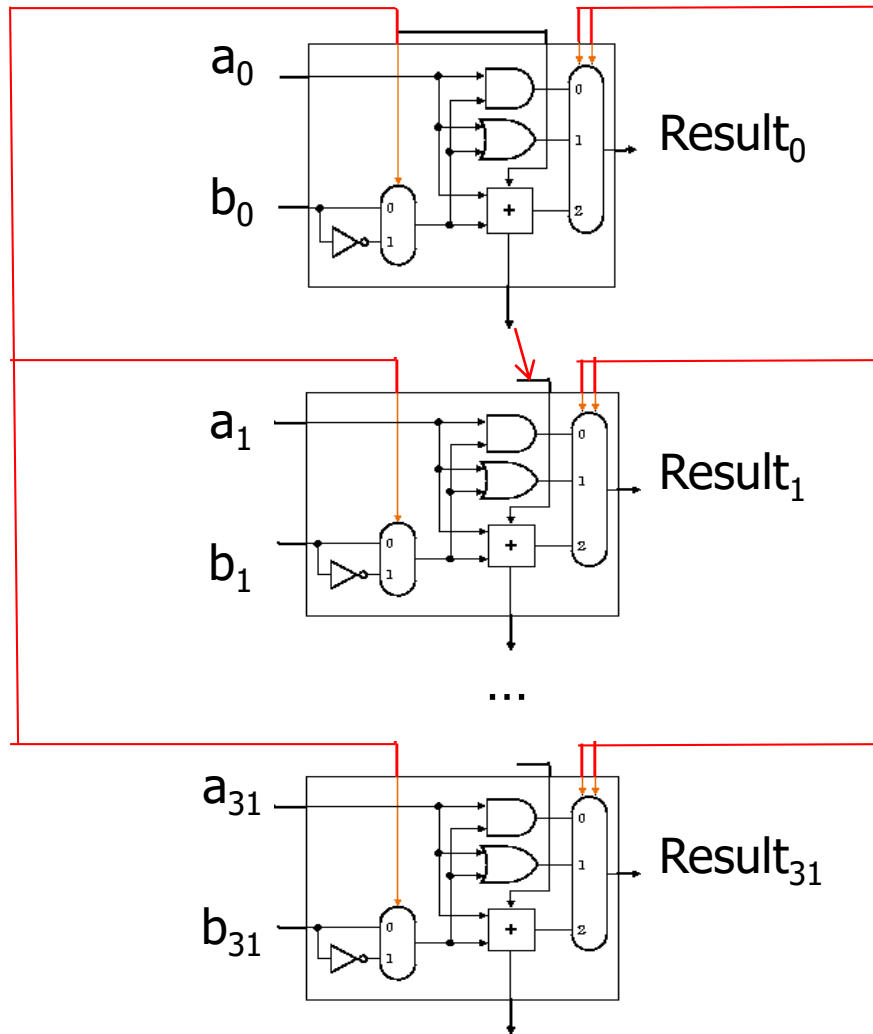
**thirty two  
1-bit ALUs  
connected  
together**


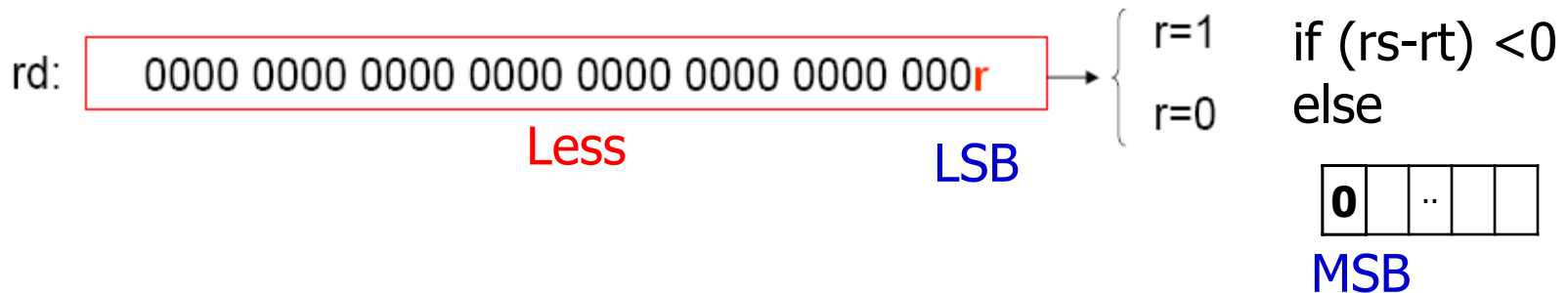
# Set on less than (slt) support

- `slt rd, rs, rt`

$$rd := \begin{cases} 1 & \text{if } (rs < rt) \\ 0 & \text{else} \end{cases}$$




[determines the sign]


- Implement the idea in ALU
  - modify 1-bit ALU for the most significant bit (ALU31 for bit 31):
    - a new output line (**Set** – 1 bit) used only for `slt`
    - (by the way we added overflow detection logic, also associated with this bit)
  - new input line (**Less** – 32 bits) goes directly to mux
  - New control line (111) for `slt`

# ALU with slt support

## LSB (ALU0)

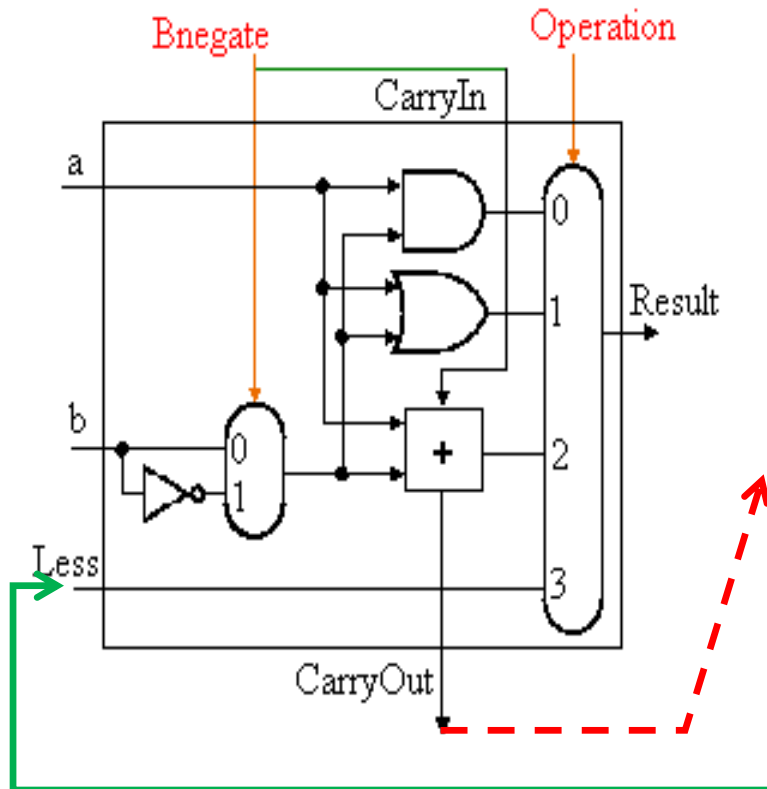

## MSB (ALU31)

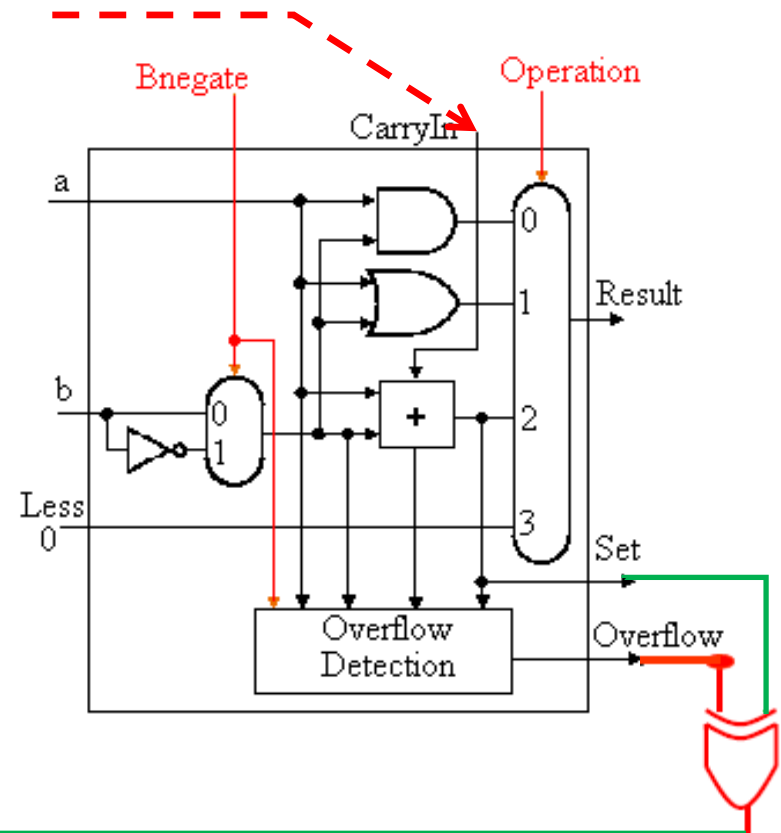




# Branch support

---


- Conditional branch instructions switch either if two registers are equal, or if they are not equal:
  - `beq register1, register2, label` (example: `beq $s4,$s2, LABEL1`)
  - `bne register1, register2, label` (example: `bne $s1,$s3, L7`)
- How to test that contents of two register is equal?
  - $a = b$  means  $(a - b) = 0$
- How to implement the above:
  - Subtract  $b$  from  $a$
  - Add hardware to test if the result is zero
    - OR all the outputs together, and invert the output:  
$$\text{Zero} = \overline{(\text{Result1} + \text{Result2} + \dots + \text{Result31})}$$
  
variable  $\begin{cases} 1 \text{ (true) if } (a - b) = 0 \text{ holds} \\ 0 \text{ (false) else} \end{cases}$
- Next slide show additional hardware for branch support :

# 32-bit ALU with branch support

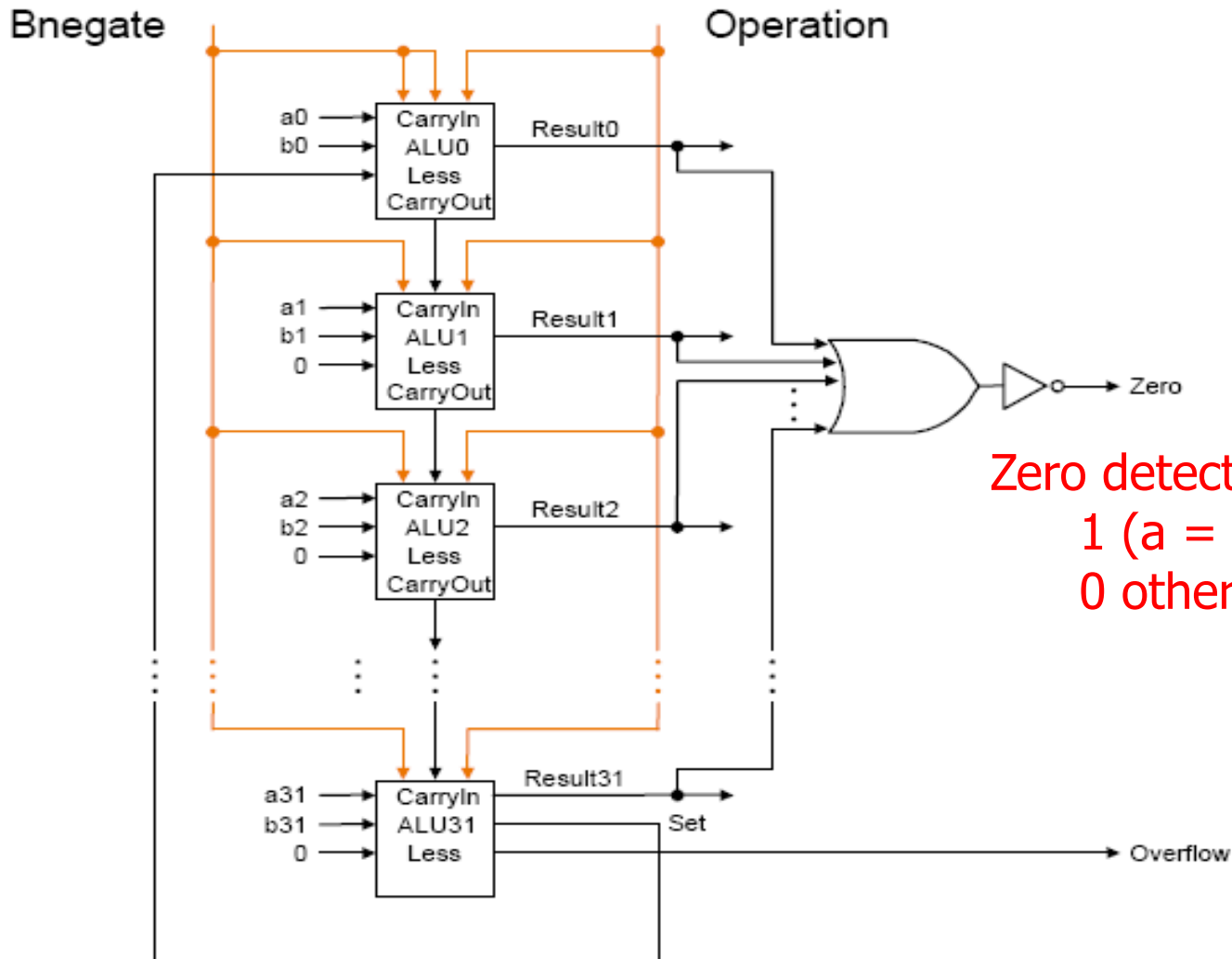
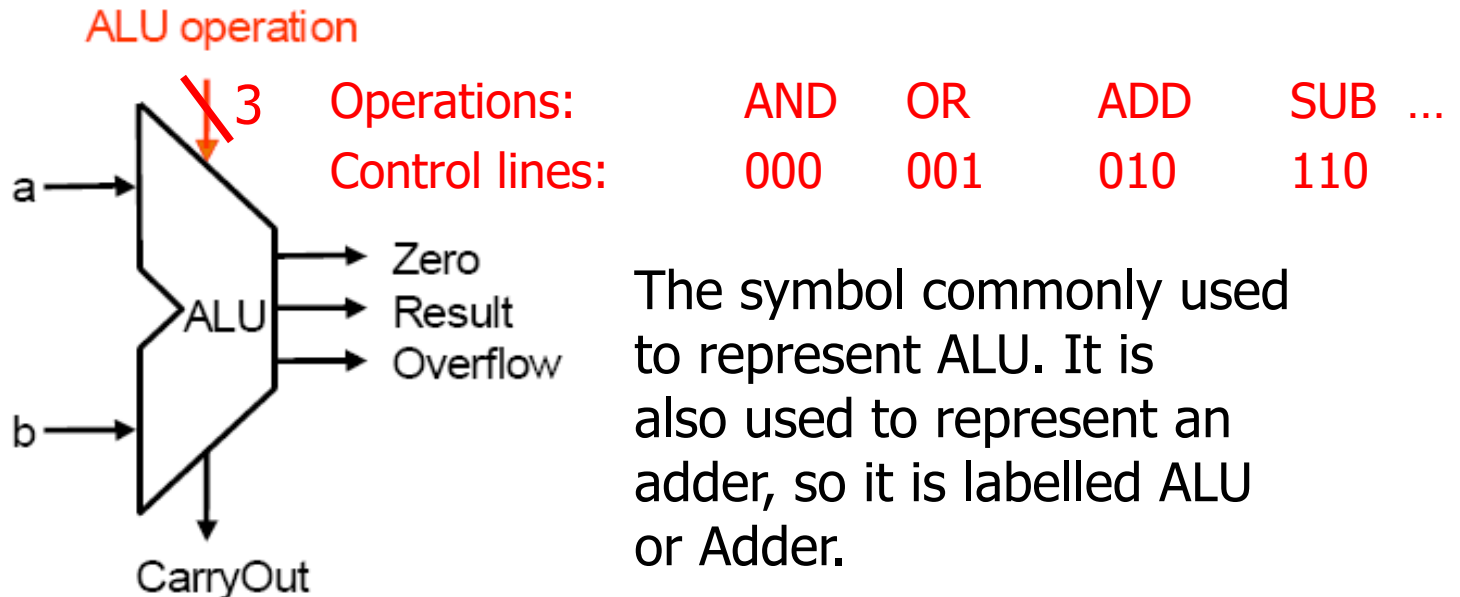
# Shift instructions


- What is left:
  - logical and arithmetic shifts *sll, srl, sra*
    - Need a new data line for a shifter (L and R)?
    - however shifters are much more easily implemented outside the ALU.
- 1-bit ALU: integrated block notation



# Revision and quiz


- Given the following Karnaugh map. The output can be expressed by  $out = c'$ .

1) True      2) False

 

- In 1-bit full Adder, the circuit construction for 'CarryOut' is correct:


1) True      2) False

 

- How ALU is used to support the branch instruction?  
beq register1, register2, label



# Recommended readings

<b>General Data</b>	<a href="#">UnitOutline</a>   <a href="#">LearningGuide</a>   <a href="#">Teaching Schedule</a>   <a href="#">Aligning Assessments</a> 
<b>Extra Materials</b>	<a href="#">ascii_chart.pdf</a>   <a href="#">bias_representation.pdf</a>   <a href="#">HP_AppA.pdf</a>   <a href="#">instruction_decoding.pdf</a>   <a href="#">masking_help.pdf</a>   <a href="#">PCSpim.pdf</a>   <a href="#">PCSpim Portable Version</a>   <a href="#">Library materials</a>

PH6: Appendix B: The Basics of Logic Design  
PH5: Appendix B: The Basics of Logic Design  
PH4: Appendix C: The Basics of Logic Design

Text readings are listed in Teaching Schedule and Learning Guide

PH6 (PH5 & PH4 also suitable): check whether eBook available on library site

PH6: companion materials (e.g. online sections for further readings)

<https://www.elsevier.com/books-and-journals/book-companion/9780128201091>

PH5: companion materials (e.g. online sections for further readings)

<http://booksite.elsevier.com/9780124077263/?ISBN=9780124077263>